## DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE

## **Regular & Supplementary Winter Examination-2023**

Semester: III

Course: B. Tech.

	Branch: Electronics and Computer Engg. / Electronics and Computer Science Engg.				
	Subject Code & Name: BTESC305 Digital Electronics and Microprocessor				
	Max Marks: 60 Date:11-	01-24 Du	ration: 3 Hr.		
	<ol> <li>Instructions to the Students:</li> <li>All the questions are compulsory.</li> <li>The level of question/expected answer as which the question is based is mentioned.</li> <li>Use of non-programmable scientific calc.</li> <li>Assume suitable data wherever necessary.</li> </ol>	in ( ) in front of the question. culators is allowed.	ome (CO) on (Level/CO)	Marks	
Q. 1	Solve Any Two of the following.		(Level/CO)	12	
A)	Perform following Conversion.		(k1/CO1)	6	
11)	a. $(0.1010)_{2} = (\dots, ?)_{10}$		(81/001)	V	
	b. $(249)_{10} = (\dots?)_{16}$				
	c. $(3241)_{8} = (\dots,?)_2$				
B)	What are the universal gates? Explain how basic	gates can be realized using	(k3/CO1)	6	
	NAND and NOR gates.				
C)	Elaborate need of coding? Explain error detection	ng and error correcting codes.	(k2/CO1)	6	
Q.2	Solve Any Two of the following.			12	
A)	Minimize following equation using Kmap  a) $F(A,B,C,D) = \sum m(0,1,2,3,4,5,13,15) + d$ b) $F(A,B,C,D) = \prod M(0,2,4,6,8,10) \cdot d(1,3,6)$		(k1/CO2)	6	
B)	Explain the working of half adder and full adder	with truth table	(k1/CO2)	6	
C)	Provide comprehensive explanation of ALU using	ng IC 74181.	(k2/CO2)	6	
Q. 3	Solve Any Two of the following.			12	
A)	Define Flip-Flop? Explain S-R Flip -Flop.		(k2/CO3)	6	
B)	Draw and explain universal shift register.		(k3/CO3)	6	
<b>C</b> )	Differentiate between synchronous counter and	asynchronous counter.	(k2/CO3)	6	
Q.4	Solve Any Two of the following.			12	
A)	Draw architecture of 8085 microprocessor and e	xplain it in detail.	(k1/CO4)	6	
B)	Explain the addressing modes of 8085 with suita	able examples of each.	(k3/CO4)	6	

C)	Write a program for addition of two 16 bit numbers using 8085. Store lower	(k2/CO4)	6		
	byte of a result at 1000H memory location and higher byte 1001H.				
Q. 5	Solve Any Two of the following.		12		
A)	Compare between 8085 and 8086 microprocessor.	(k1/CO5)	6		
B)	Describe 8086 flag register and its functions.	(k3/CO5)	6		
C)	Explain hardware and software interrupts of 8086.	(k2/CO5)	6		

\*\*\* End \*\*\*